

GUJARAT TECHNOLOGICAL UNIVERSITY**BE- SEMESTER-I&II EXAMINATION – SUMMER 2025****Subject Code:3110005****Date:01-07-2025****Subject Name:Basic Electrical Engineering****Time:10:30 AM TO 01:00 PM****Total Marks:70****Instructions:**

1. Attempt all questions.
2. Make suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Simple and non-programmable scientific calculators are allowed.

Q.1	(a) State Ohm's law and Kirchhoff's laws.	03
	(b) Define power factor. Write the disadvantages of low power factor.	04
	(c) Derive the equation of star to delta and delta to star transformation.	07
Q.2	(a) Write the advantages and disadvantages of polyphase systems.	03
	(b) Define: (i) Form factor (ii) Peak factor (iii) Frequency and (iv) Cycle.	04
	(c) State and explain Thevenin's theorem with suitable example.	07
	OR	
	(c) A 100 V, 100-Watt lamp is connected in series with a 100 V, 60-watt lamp across 200 V supply. Determine current drawn and power consumed by each lamp.	07
Q.3	(a) Define: (i) Active power (ii) Reactive power and (iii) apparent power in ac circuits.	03
	(b) Explain the comparison between series resonance and parallel resonance condition in ac circuits.	04
	(c) Prove that current in purely inductive circuit lags its voltage by 90 degree and average power consumption in pure inductive circuit is zero.	07
	OR	
Q.3	(a) Define and explain RMS value and average value in ac circuits.	03
	(b) Derive an expression for impedance, current and power factor for an R-L-C series circuit when supplied with ac voltage. Also draw the phasor diagram.	04
	(c) Derive the relationship between line voltage and phase voltage, line current and phase current in a 3-phase balanced star connected circuit	07
Q.4	(a) Define transformer. Write the main parts of transformer.	03
	(b) Compare auto transformer with two winding transformers.	04
	(c) Explain various connections of 3-phase transformers with necessary diagrams.	07
	OR	
Q.4	(a) Write the advantages and disadvantages of auto transformer.	03
	(b) Write the types of 1-phase induction motors. Explain any one of them.	04
	(c) Explain construction and working of synchronous generator with necessary diagram.	07
Q.5	(a) Compare squirrel cage induction motor with slip ring induction motor.	03
	(b) Explain the types of dc motors with diagrams.	04
	(c) Define earthing. Explain plate earthing with diagram.	07
	OR	
Q.5	(a) Give a list of safety devices used for home appliances.	03
	(b) Write the comparison of Fuse, MCB and ELCB.	04
	(c) A series R-L-C circuit having a resistance of 8Ω , inductance of 80 mH and capacitance of $100 \mu\text{F}$ is connected across a 150 Volt, 50 Hz supply. Calculate (i) the current (ii) the power factor and (iii) the voltage drops in the coil and capacitance.	07
